

## 1) Hand Calculation

A)

V <sub>CC</sub>	R <sub>in</sub> *	A <sub>i</sub> *
20V	4018.65Ω	200.54

B)

I <sub>CQ</sub>	V <sub>BEQ</sub>	V <sub>CEQ</sub>	P <sub>D</sub>
2.4mA	0.7V	17.5	42mW

C) I<sub>ps1</sub> (Project #1 and #2) = 186mA

I<sub>ps2</sub> (Project #3) = 4.8mA


I<sub>ps (Total)</sub> = 186mA + 4.8mA = 190.8mA

D)

A <sub>i</sub> (Project #3)	A <sub>i</sub> (Project #1, 2)	A <sub>i</sub> (Total)
49.87	200.54	1000

E)


R<sub>in</sub> = 216nΩ

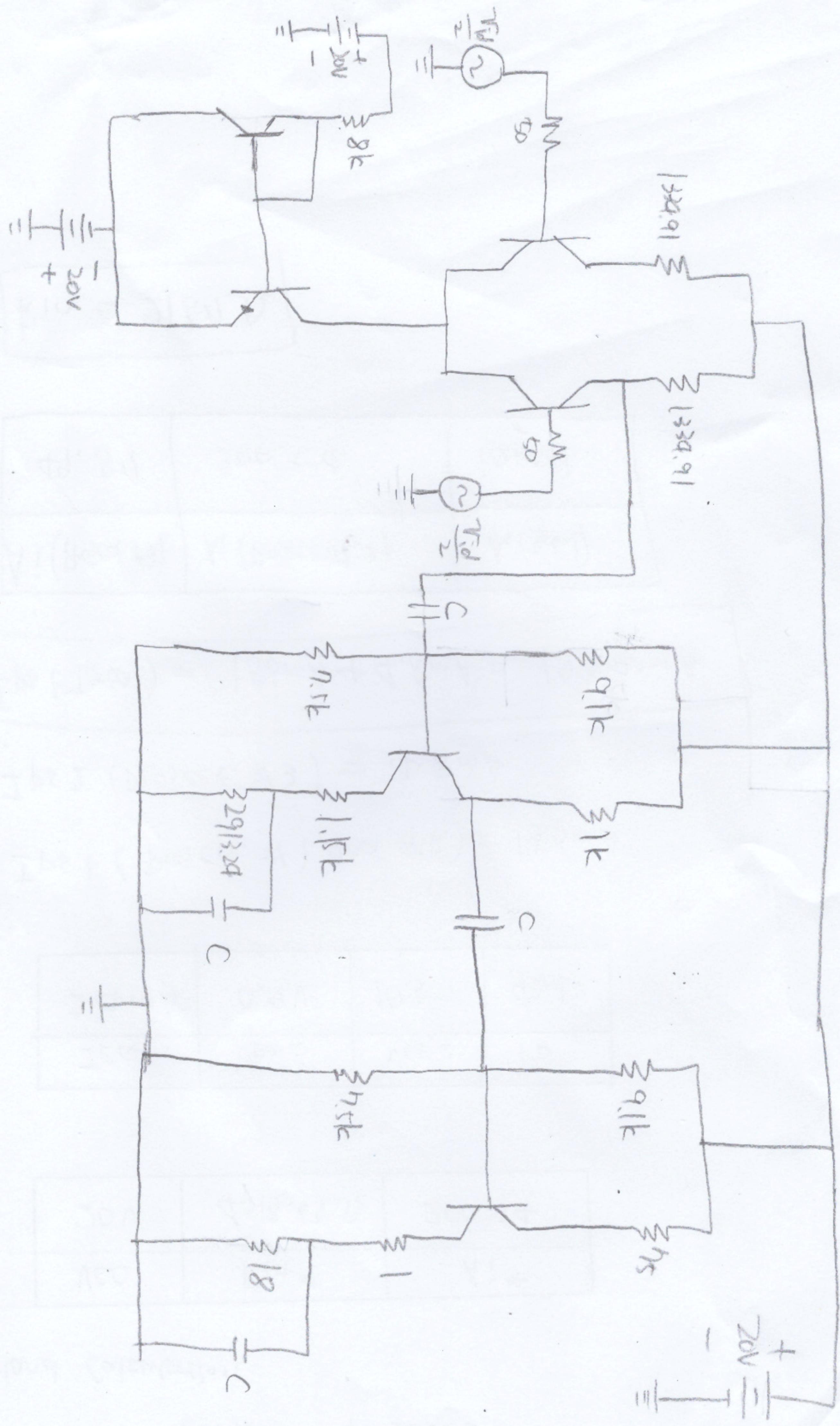

$$G) A_i^* = 200.54 \quad , \quad \beta = 200$$

$$\Rightarrow \text{Current gain of Driver Amp} = 10000 / 200.54 = \boxed{49.87}$$

Differential-pair Small signal

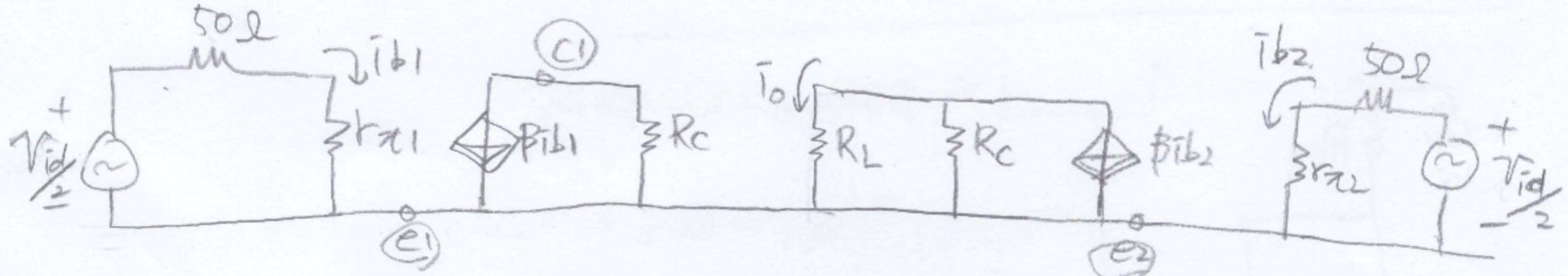

$$\textcircled{1} \text{ KVL @ } e \quad (e_1 = e_2)$$

$$(1 + \beta) i_b1 + (1 + \beta) i_b2 = 0$$

$$\Rightarrow i_b1 = -i_b2$$

$$\bar{i}_{in} = i_b1, \quad i_o = \beta i_b2 \left( \frac{R_c}{R_c + R_L} \right)$$

$$\Rightarrow A_i = \frac{i_o}{\bar{i}_{in}} = \frac{\beta i_b2 \left( \frac{R_c}{R_c + R_L} \right)}{i_b1} = \frac{\beta i_b2 \left( \frac{R_c}{R_c + R_L} \right)}{-i_b2} = -\beta \left( \frac{R_c}{R_c + R_L} \right) = 49.87$$

$$\Rightarrow -200 \left( \frac{R_c}{R_c + R_L} \right) = 49.87$$

$$\Rightarrow \frac{R_c}{R_c + R_L} = -0.2991 = 0.249 \quad R_L = R_{in}^* = 4018.65 \Omega$$

$$\Rightarrow \frac{R_c}{R_c + 4018.65} = 0.249 \Rightarrow \boxed{R_c = 1334.91}$$

DC Analysis (Differential-pair)

$$Q_1, Q_2 \text{ matched} \Rightarrow I_{S1} = I_{S2}, \quad \beta_1 = \beta_2$$

$$\Rightarrow i_{C1} = i_{C2} \text{ and } i_{E1} + i_{E2} = I_{DC}$$


$$V_{B1} = V_{B2} = \phi V$$

$$V_{E1} = V_{E2}$$

$$\Rightarrow V_{BE1} = V_{BE2}$$

$$\Rightarrow I_{E1} = \frac{I_C1}{\alpha} = \frac{I_C2}{\alpha} = I_{E2} \Rightarrow I_{E1} = I_{E2} = \frac{I_{DC}}{2}$$

### Basic current Mirror (DC Analysis)

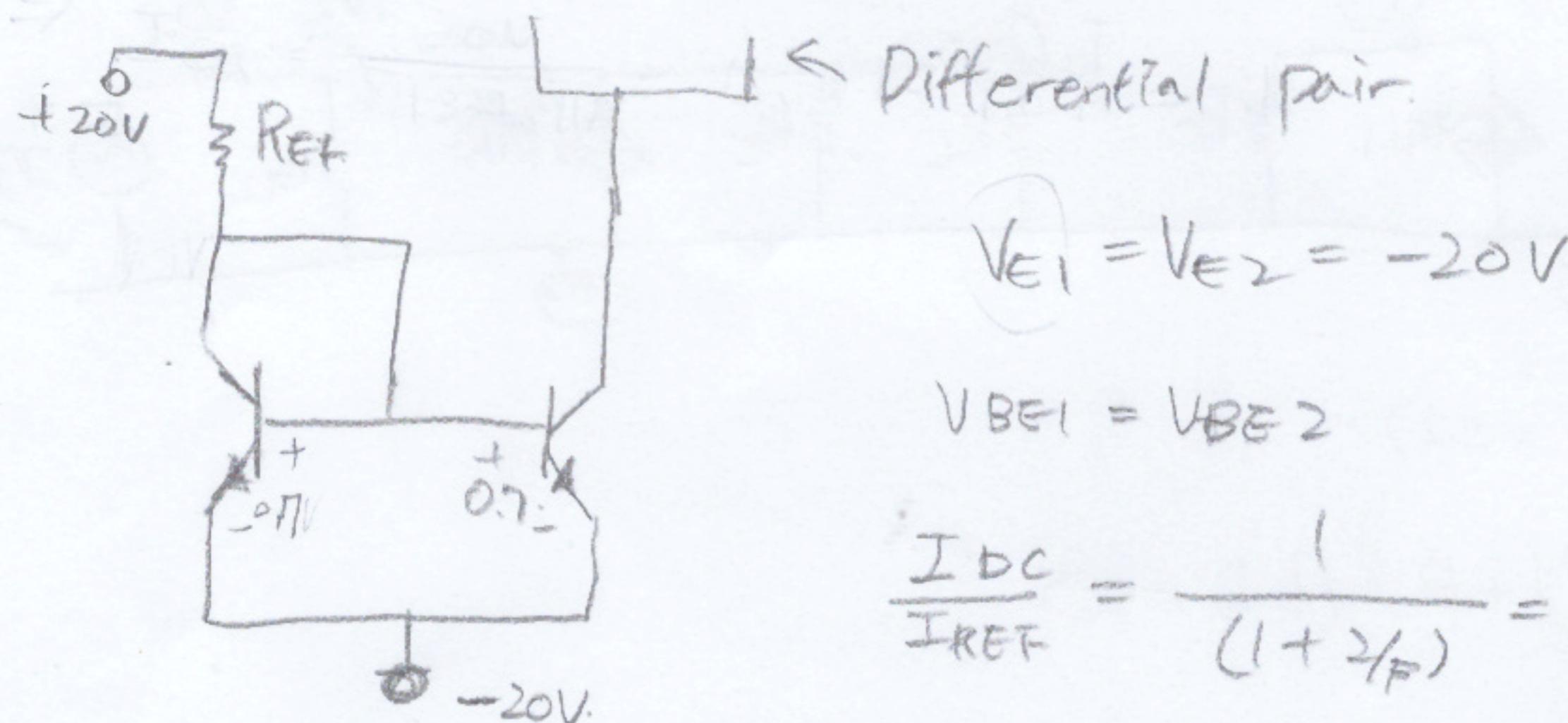

$$\frac{I_{DC}}{I_{REF}} = \frac{1}{(1+2/\beta)} = \frac{1}{1+\frac{1}{50}} = \frac{1}{1.02}$$

$$I_{DC} = I_{REF} \left( \frac{1}{1.02} \right) \quad V_{CC} = 20V, \quad V_{EE} = -20V$$

$$\text{Let } R_{REF} = 8k\Omega, \quad V_{BE} = 0.7V$$

$$\Rightarrow \frac{20 - 0.7 - (-20)}{8k} = \frac{39.5V}{8000\mu A} = 0.004945 = 4.945mA$$

$$\Rightarrow I_{DC} = 4.945 \left( \frac{1}{1.02} \right) = 4.819mA$$

### Differential pair (DC pair)

$$I_{E1} = \frac{I_{DC}}{2} = \frac{4.819mA}{2} = 2.41mA = I_{E2}$$

$$I_C1 = I_C2 = \frac{\beta}{\beta+1} 2.41 = \frac{200}{201} (2.41) = 2.4mA$$

$$\Rightarrow I_{PS} = I_{C1} + I_{C2} = 4.8mA$$

$$V_{C1} = V_{C2} = V_{CC} - R_C I_{C1} = 20 - 1334.91 \text{ (2.4mA)} \\ = 16.8V$$

$$V_{E1} = V_{E2} = -0.7V$$

$$\Rightarrow V_{CE} = 16.8 - (-0.7V) = 17.5V$$

$V_{CEQ} = 17.5V$   
Forward Active

### AC Analysis

$$A_i = 49.87 \quad \text{and} \quad A_{i^*} = 200.54 \quad (\text{project #1 and #2})$$

$$\Rightarrow A_i(\text{total}) = (A_i)(A_{i^*}) = (49.87)(200.54) = 10001$$

$A_i(\text{total}) = 10001$

$$R_{in} = \frac{V_{in}}{I_{in}} \quad [i_{in} = i_b] \quad i_b = \frac{V_{in} - V_e}{50 + r_{\pi}} = \frac{V_{in}}{50 + r_{\pi}}$$

$$r_{\pi} = \frac{\beta V_t}{I_{CQ}} = \left( \frac{200(26mV)}{2.4mA} \right) = 2167\Omega$$

$$R_{in} = \frac{V_{in}}{\left[ \frac{V_{in}}{2167\Omega} \right]} = 2167\Omega$$


$\therefore R_{in} = 2167\Omega$

$$P_D = (V_{CEQ})(I_{CQ}) = (7.5V)(2.4mA) = 0.042$$


$$= 42mW$$

$$\therefore \boxed{P_D = 42mW}$$

2

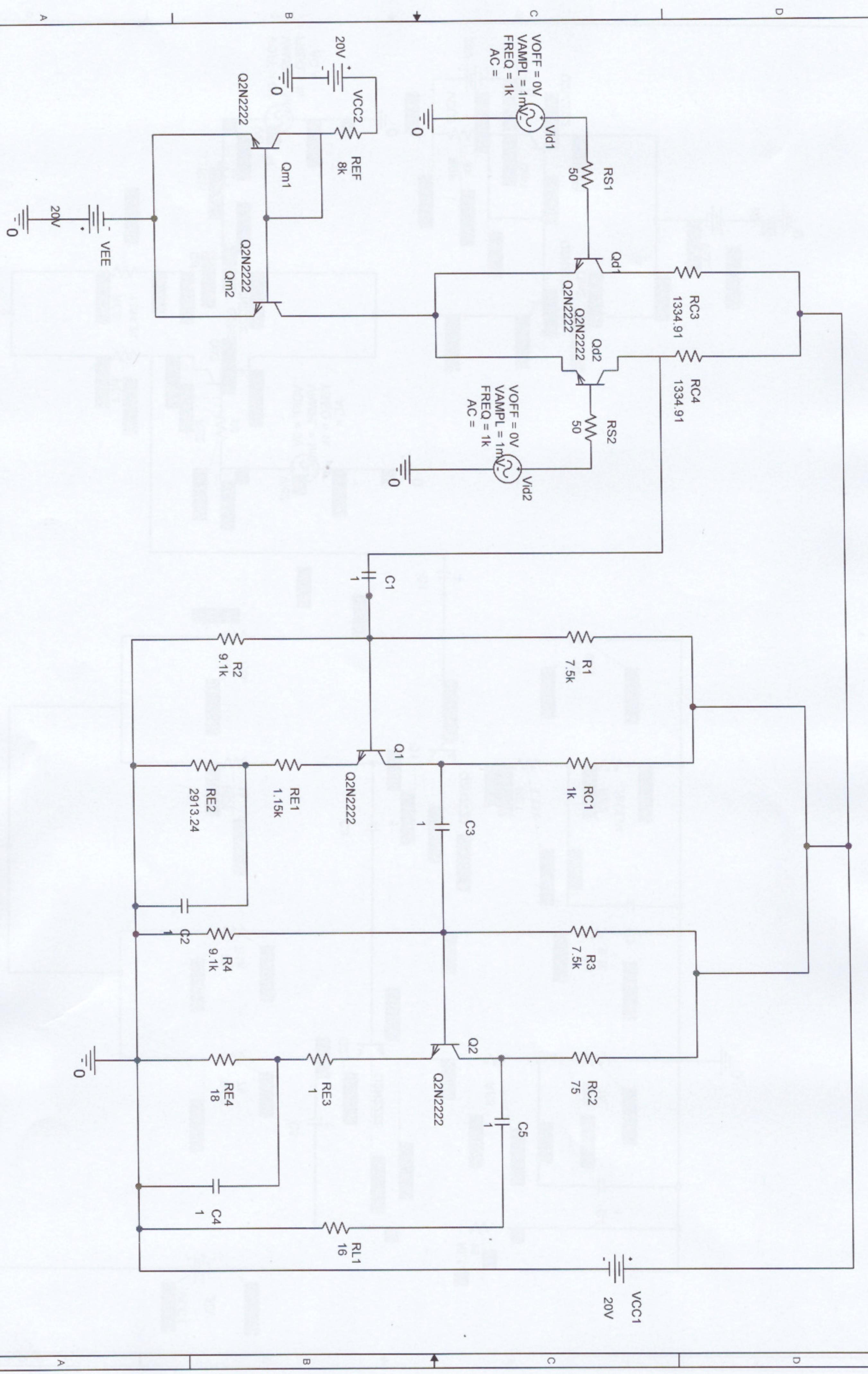

A)

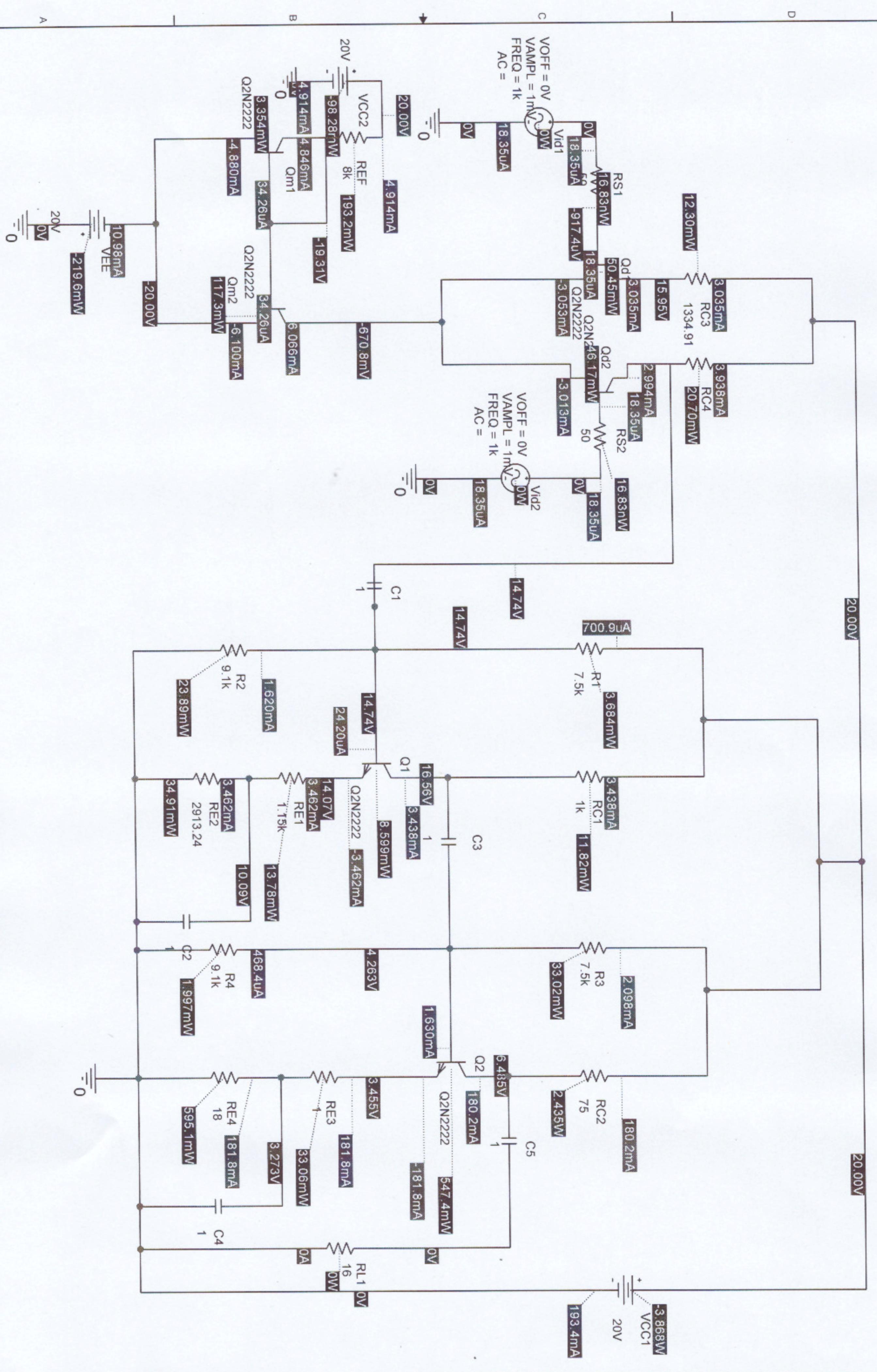

### PSpice part

#### B) SIMULATED DC BIAS

(Project#1 and #2)

Simulated value (project # 1)	
ICQ	180.2mA
VCEQ	3.03V
VBEQ	0.808V
$P_D$ ,transistor	547.4mW
Simulated value (project #2)	
ICQ	3.438mA
VCEQ	2.49V
VBEQ	0.67V
$P_D$ ,transistor	8.599mW

#### Project#3


Simulated value		Hand-calculated value	
ICQ	3.035mA	ICQ	2.4mA
VCEQ	16.62V	VCEQ	17.5V
VBEQ	0.7V	VBEQ	0.7V
$P_D$ ,transistor	46.17mW	$P_{DS}$ ,transistor	42mW

#### C) SIMULATED POWER SUPPLY BIAS


DC power Supply Current (Ips) = 193.4mA.
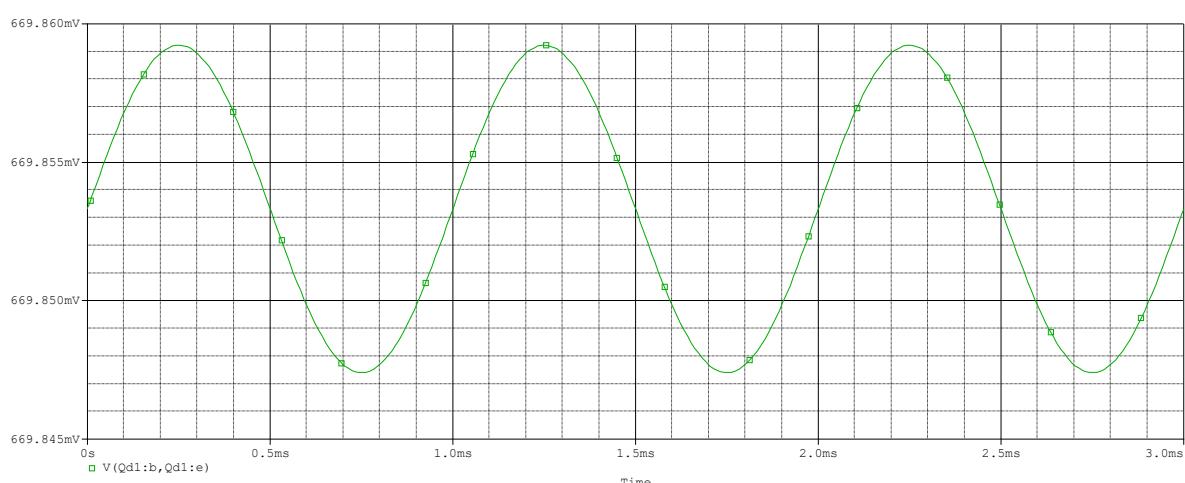
#### D) SIMULATED SMALL SIGNAL OPERATION

The amplitude value of the source voltage for small signal operation is 20mV for all transistors.


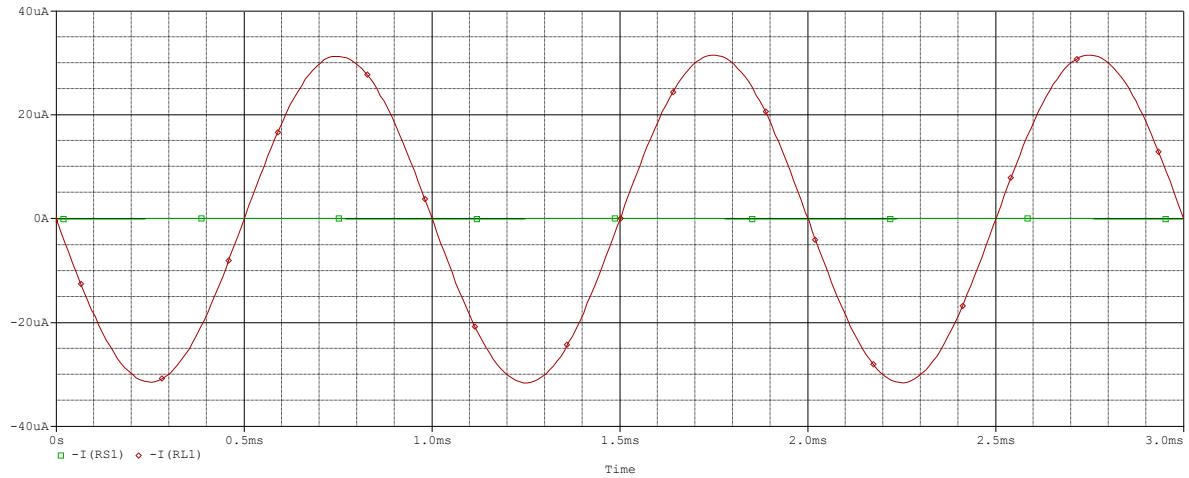
### E) SIMULATED TWO-STAGE CURRENT GAIN ( $\beta=200$ )



$$\beta = 200, A_i = \frac{31.430\mu A}{2.84nA} = 11066.9$$

I almost achieve a current gain variation 10% about the nominal value of  $\beta = 200$ .

### F) SIMULATED INPUT RESISTANCE

$$\beta = 200, R_{in} = \frac{10.908mV}{5.177\mu A} = 2017.01\Omega = 2k\Omega$$

The input resistance is not greater than  $20k\Omega$ .