

## EE 3124 Project #2

Design a two-stage BJT class-A amplifier to provide the following characteristics.

Jaeha Huh

Design a two-stage BJT class-A amp.

A) 1) Hand Calculations:

$V_{CC}$	$R_{in}^*$	$A_i^*$
20V	103.66Ω	63.99

$$\beta = 200$$

From project #1

B)

$I_{CQ}$	$V_{BEQ}$	$V_{CEQ}$	$P_D$
180.2mA	0.808V	3.03V	547.4mW

Project #1

Power-amp stage

$I_{CQ}$	$V_{BEQ}$	$V_{CEQ}$	$P_D$
2.5mA	0.7V	7.3V	18.25mW

Project #2

driver stage

C) Power rating for each resistors

$R_1$	$R_2$	$R_C$	$R_{E1}$	$R_{E2}$
10.9mW	13.2mW	6.25mW	7.245mW	18.35mW

$$I_{ps1} (\text{Project #1}) = 182.298 \text{ mA}$$

$$I_{ps2} (\text{Project #2}) = I_{R1} + I_{CQ} = 1.205 \text{ mA} + 2.5 \text{ mA} \\ = 3.705 \text{ mA}$$

$$\therefore I_{ps(\text{Total})} = I_{ps1} + I_{ps2} = 186.003 \text{ mA} \approx 186 \text{ mA}$$

E)

$A_i$ (driver stage)	$A_i$ (Power amp stage)	$A_i$ (Total)
3.139	63.99	200.86


$$A_i(\text{Total}) = A_i(\text{driver}) \times A_i(\text{Power amp}) = 3.139 \times 63.99$$

$$A_i(\text{Total}) = 200.86 \approx 201$$

F)

$R_{in} = 4040.23\Omega$
--------------------------

It is less than  $10k\Omega$ .

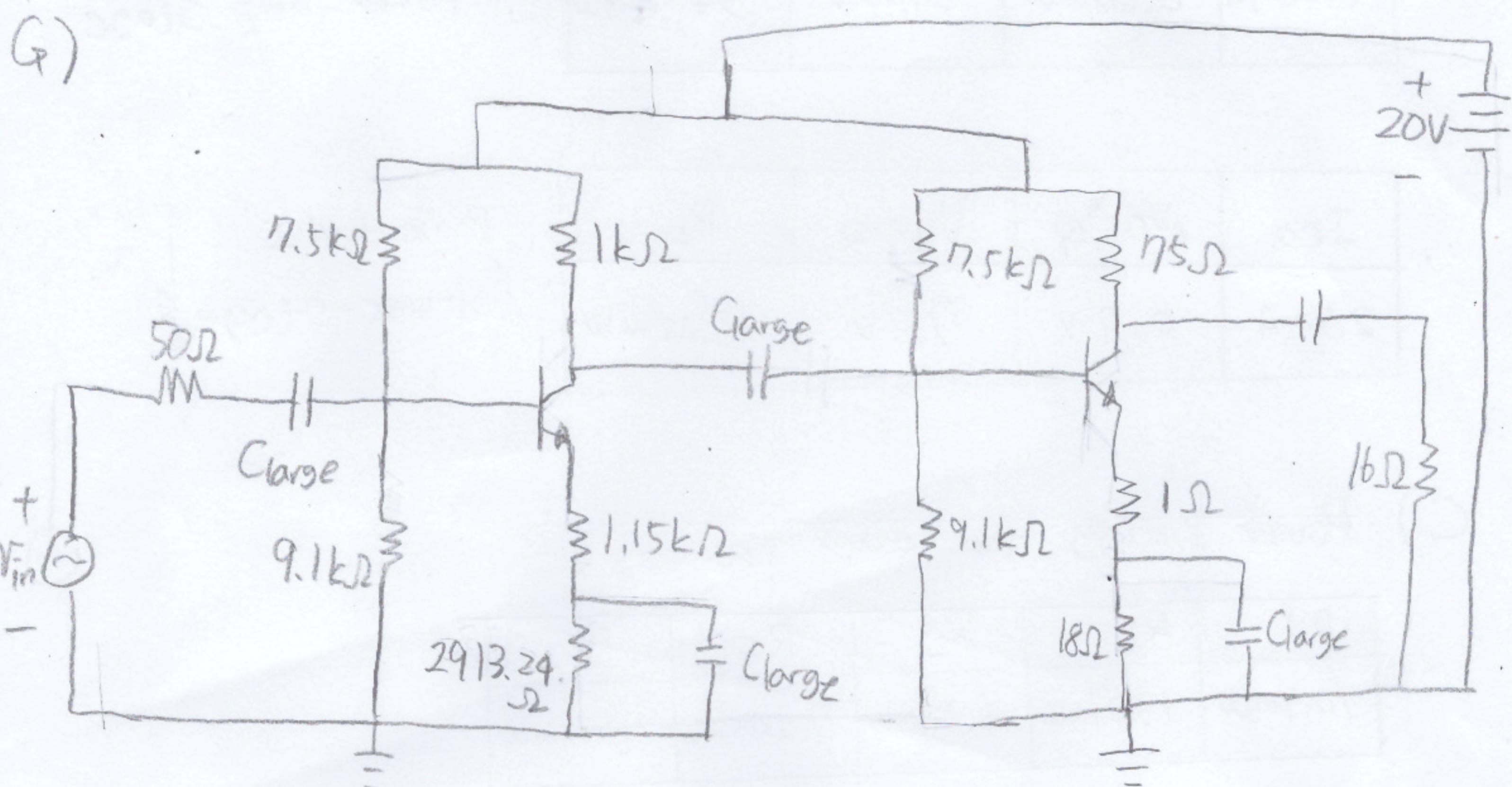

## H) Hand Calculation for Driver stage.

Given: From project 1, we know  $A_i^* = 63.99$

$$\Rightarrow \text{Max (peak) current swing of Driver Amp} = 125\text{mA}/(A_i^*) \\ = \frac{125\text{mA}}{63.99} = 1.9534 \text{ mA}$$

So, let  $I_{C,\text{peak}} = 3.5 \text{ mA}$  and  $R_L = R_{in}^* = 103.66 \Omega$  (given)

$$\Rightarrow I_{L,\text{peak}} = I_{C,\text{pk}} - \frac{R_c}{R_c + R_L} \quad ; \text{let } R_c = 1k$$


$$I_{L,\text{pk}} = 3.5 \text{ mA} \cdot \frac{1k}{1k + 103.66} = 3.171 \text{ mA}$$

So,  $I_{L,\text{pk}} = 3.171 \text{ mA}$  (my assumption)  $> 1.9534 \text{ mA}$  (calculation)

$$\Rightarrow \text{let } I_{CQ} = 3.171 \text{ mA.} = 0.003171 \text{ A}$$

by formula of  $I_{CQ}$  with Max swing
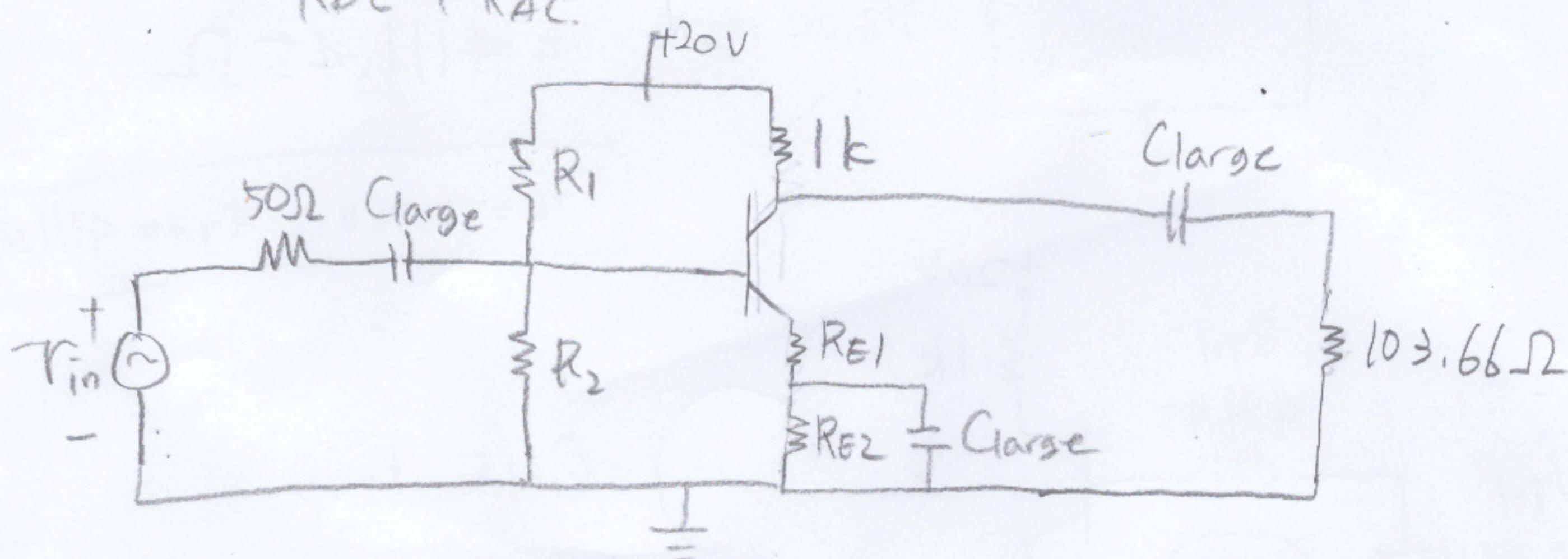
$$I_{CQ} = \frac{V_{CC}}{R_{DC} + R_{AC}} \quad V_{CC} = 20 \text{ V (given)}$$



$$0.003171 = \frac{20}{R_{DC} + R_{AC}} \Rightarrow R_{DC} + R_{AC} = \frac{20}{0.003171}$$

$$\Rightarrow R_{DC} + R_{AC} = 6307.16 \Omega$$

(B)

$$R_{DC} = R_C + R_{E1} + R_{E2} \rightarrow R_{AC} = (R_C || R_L) + R_{E1}$$

$$R_{DC} + R_{AC} = R_C + 2R_{E1} + R_{E2} + R_C || R_L = 6307.16$$


$$2R_{E1} + R_{E2} = 5213.24$$

Let  $R_{E1} = 1.15k\Omega$ , then  $R_{E2} = 2913.24\Omega$

$\Rightarrow [R_C = 1k\Omega, R_{E1} = 1.15k\Omega, R_{E2} = 2913.24\Omega]$

Pick  $R_1 = 7.5k$  and  $R_2 = 9.1k$  (from standard resistance value)


### DC Analysis

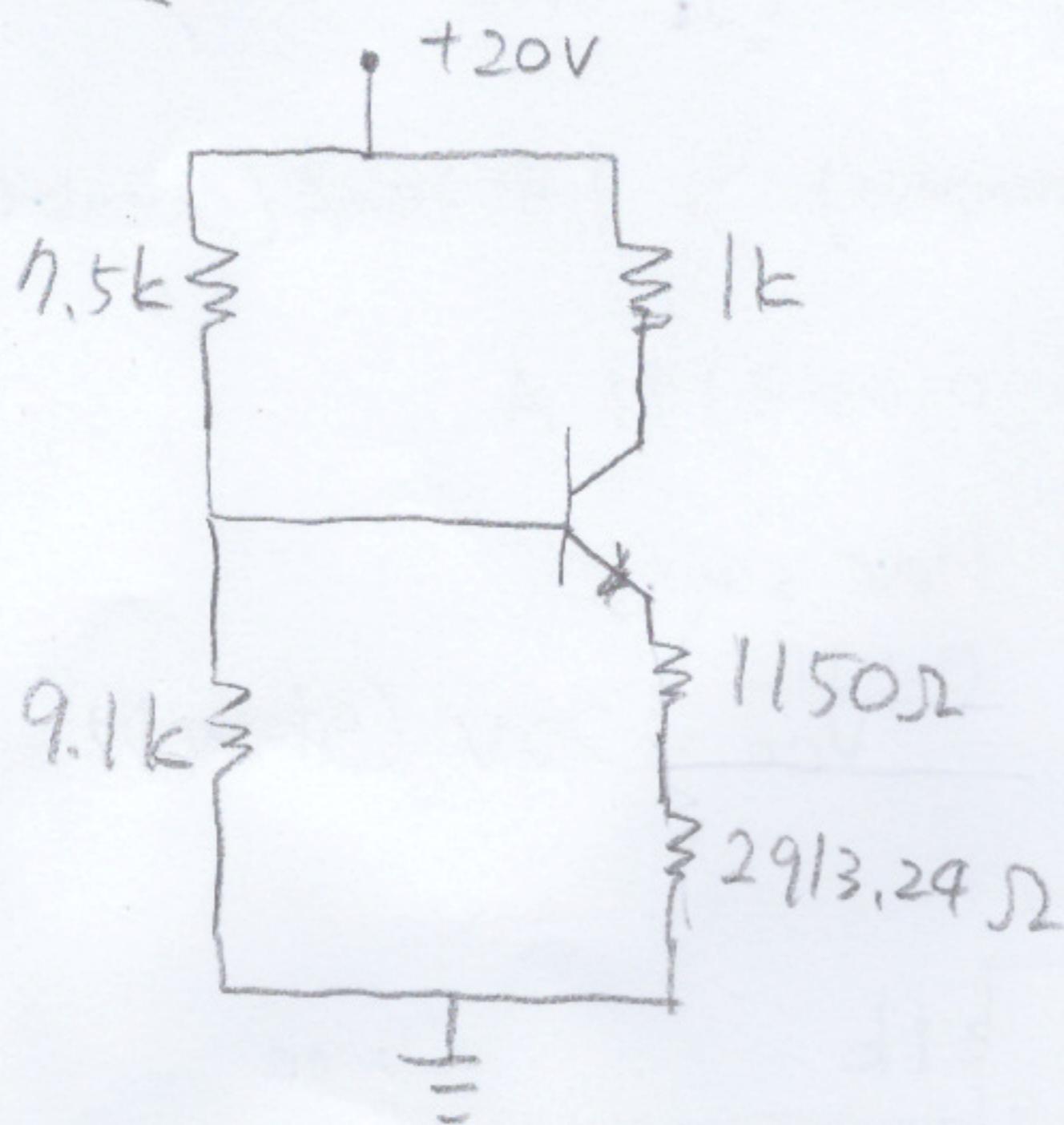

$$V_{TH} = 20V \left( \frac{9.1k}{16.6k} \right) = 10.96V$$

$$\begin{aligned} R_{TH} &= R_1 || R_2 \\ &= \frac{9.1k \times 7.5k}{16.6k} \\ &= 4111.45\Omega \end{aligned}$$

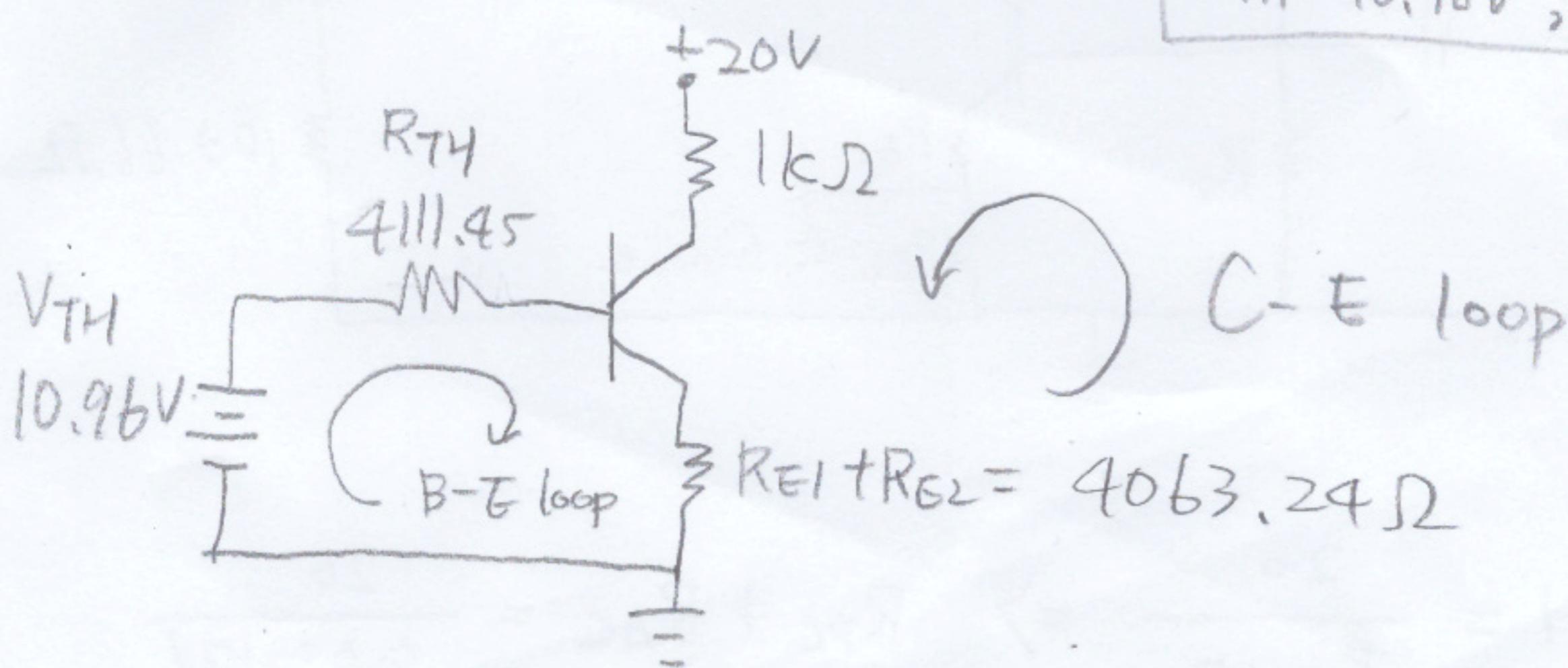$V_{TH} = 10.96V, R_{TH} = 4111.45\Omega$



$$R_{E1} + R_{E2} = 4063.24\Omega$$

① KVL: B-E Loop

$$0 = -V_{TH} + R_{TH}(I_{BQ}) + V_{BEQ} + (4063.24)(I_{EQ})$$

$$I_{EQ} = (\beta + 1) I_{BQ} \quad \beta = 200 \text{ (given)}$$

$$0 = -V_{TH} + R_{TH}(I_{BQ}) + V_{BEQ} + (4063.24)(\beta + 1) I_{BQ}$$

$$0 = -10.96 + (4111.45)(I_{BQ}) + 0.7 + (4063.24)(201) I_{BQ}$$

$$I_{BQ} = \frac{10.96 - 0.7}{820822.7} = \frac{10.26}{820822.7} = 0.0000125 = 12.5 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 200 (12.5 \text{ mA}) = 2.5 \text{ mA}$$

$$I_{EQ} = (\beta + 1) I_{BQ} = 201 (12.5 \text{ mA}) = 2.51 \text{ mA}$$

$$\rightarrow \boxed{I_{BQ} = 12.5 \text{ mA}, I_{CQ} = 2.5 \text{ mA}, I_{EQ} = 2.51 \text{ mA}}$$

② KVL: C-E Loop

$$0 = -V_{CC} + R_C(I_{CQ}) + V_{CE} + R_E(I_{EQ})$$

$$V_{CE} = V_{CC} + R_C(I_{CQ}) - R_E(I_{EQ})$$

$$= 20 - 1k(2.5 \text{ mA}) - (4063.24)(2.51 \text{ mA})$$

$$= 20 - 2.5 - 10.2 = 7.3 \text{ V}$$

$$V_{CEQ} = 7.3 \text{ V} > V_{CE, \text{ Sat}} = 0.3 \text{ V}$$

$$\therefore \boxed{V_{CEQ} = 7.3 \text{ V}}$$

Forward Active

$$\textcircled{3} \quad P_D \approx (V_{CEQ}) (I_{CQ}) = (7.3V)(2.5mA)$$

$$= 0.01825 = \underline{18.25mW}$$

$$\therefore \boxed{P_D = 18.25mW}$$

$$P_{RC} = I^2 R = (I_{CQ})^2 (R_C) = (2.5mA)^2 (1k\Omega) = 6.25mW$$

$$P_{RE1} = (R_{E1}) (I_{EQ})^2 = (1.15k) (2.51mA)^2 = 7.245mW$$

$$P_{RE2} = (R_{E2}) (I_{EQ})^2 = (2913.24) (2.51mA)^2 = 18.35mW.$$

$$\textcircled{4} \quad V_{RI} = V_{cc} - V_B = 20 - 10.96 = 9.04$$

$$I_{RI} = \frac{V_{RI}}{R_1} = \frac{9.04}{7.5k} = 1.205mA$$

$$\boxed{I_{RI} = 1.205mA}$$

$$\Rightarrow P_{RI} = (R_1) (I_{RI})^2 = 10.9mW$$

$$I_{RI} = I_{R2}$$

$$\Rightarrow P_{R2} = (R_2) (I_{R2})^2 = 13.21mW$$

$\therefore$  Power dissipation of resistors

$$\Rightarrow \boxed{\begin{aligned} R_1 &= 10.9mW & R_2 &= 13.21mW & R_C &= 6.25mW \\ R_{E1} &= 7.245mW & R_{E2} &= 18.35mW \end{aligned}}$$

\textcircled{6}

$$\textcircled{4} \quad r_o = \infty$$



$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{200(26\text{mA})}{(2.5\text{mA})} = 2080$$

$$g_m = \frac{\beta}{r_\pi} = \frac{200}{2080} = 0.096$$

$$\therefore \boxed{r_\pi = 2080, g_m = 0.096}$$

## Ac Analysis

### ① Small signal

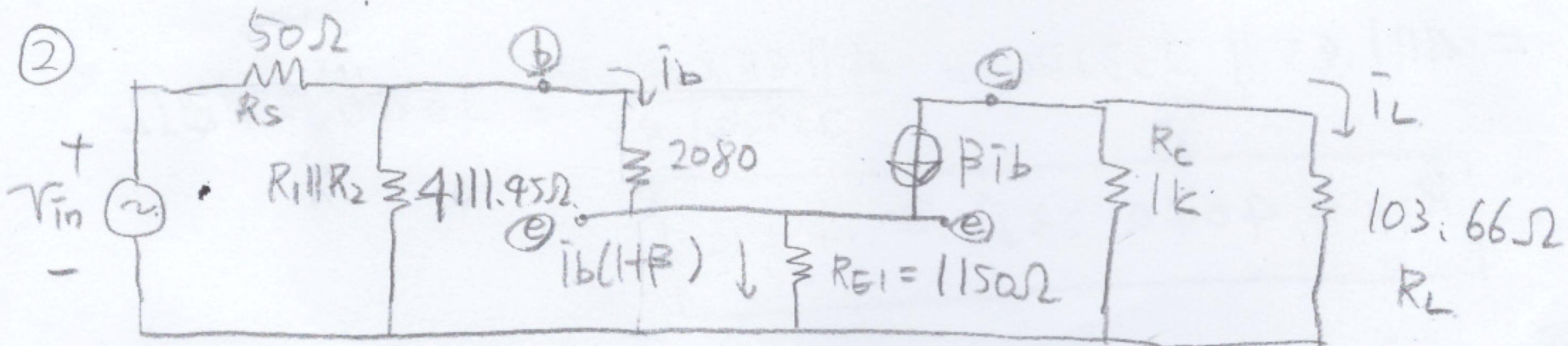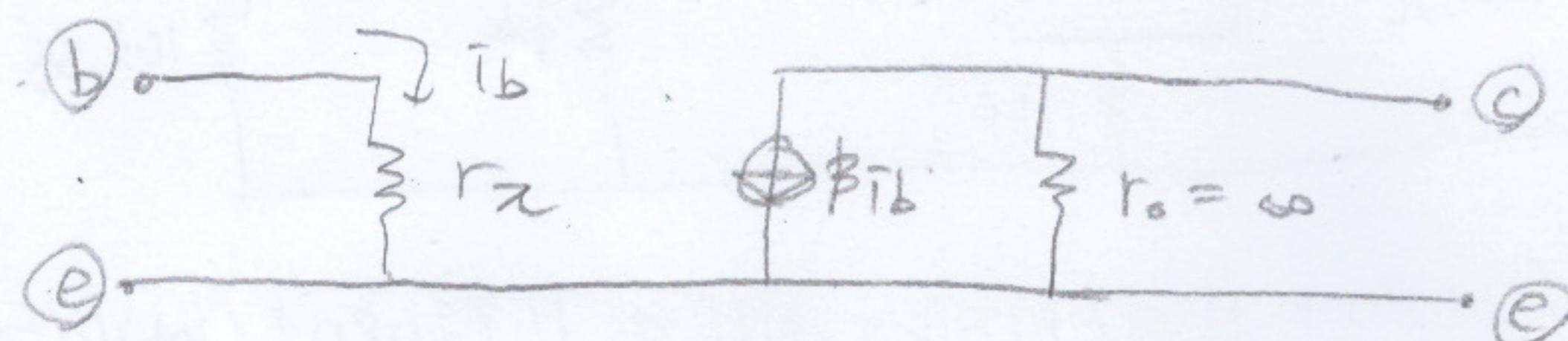

$$\text{Current gain of Driver Amp} = 200 / A_i^* = \frac{200}{63.99} = 3.1255$$

(This is primary goal)  $\therefore A_i(\text{goal}) = 3.1255$

### Hand Calculation:

$$2080 + (201) 1150 = 233230 \Omega$$

$$i_b = i_{in} \left( \frac{4111.45}{4111.45 + 233230} \right) \Rightarrow i_{in} = \frac{237341.45}{4111.45} i_b$$

$$\Rightarrow i_b = 57.727$$

⑦

$$\bar{i}_o = -\beta i_b \left( \frac{1k}{1k+103.66} \right) = -200 \left( \frac{1k}{1k+103.66} \right) \bar{i}_b$$


$$\bar{i}_o = -181.215$$

$$\therefore A_i = \left| \frac{\bar{i}_o}{\bar{i}_{in}} \right| = \left| \frac{-181.215}{57.727} \right| = 3.139$$

$$\boxed{A_i = 3.139}$$

$\Rightarrow A_i$  (by hand calculation)  $\approx A_i$  (goal).


$$3.139 \approx 3.1255.$$

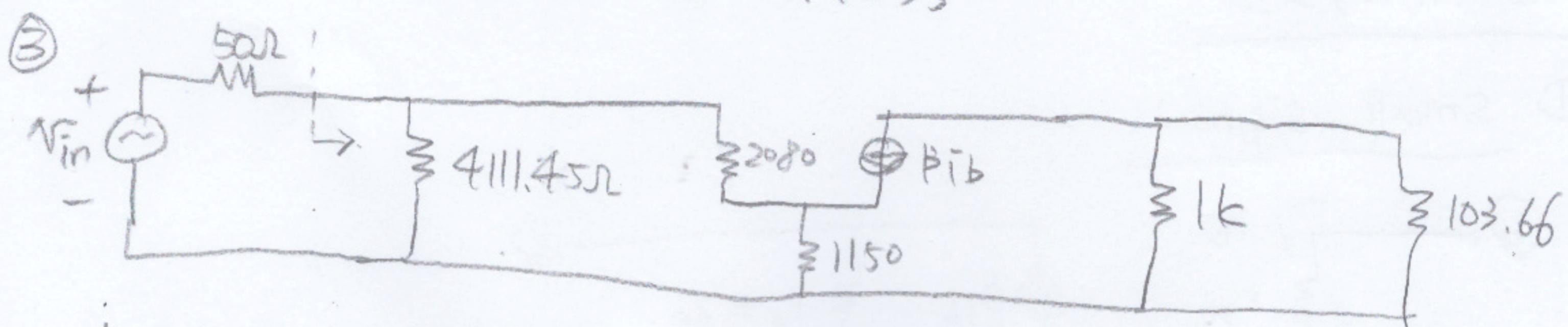

$$\begin{aligned} R_{in} &= 4111.45 \parallel (2080 + 1150(1+\beta)) = 4111.45 \parallel (2080 + (201)(1150)) \\ &= 4111.45 \parallel 233230 = \frac{4111.45 \times 233230}{237341.45} = 4040.228\Omega \end{aligned}$$

$$\boxed{R_{in} = 4040.23\Omega \approx 4k\Omega}$$

(4)  $R_o = \frac{V_x}{i_x} \Big|_{V_{in}=0}$

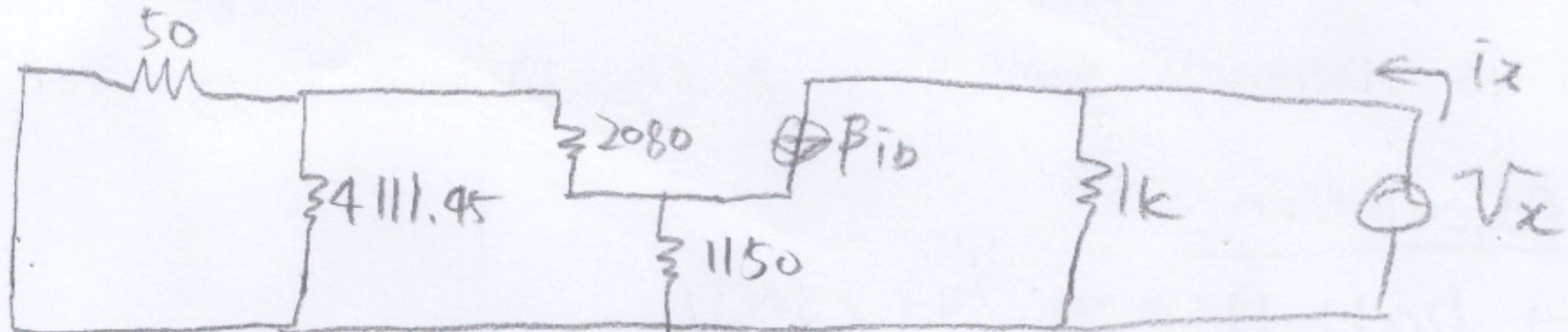


$$\bar{i}_b = 0, \beta \bar{i}_b = 0 \Rightarrow V_x = i_x 1k$$

$$\boxed{R_{out} = 1k\Omega}$$

(8)

A) PSPice Schematic.

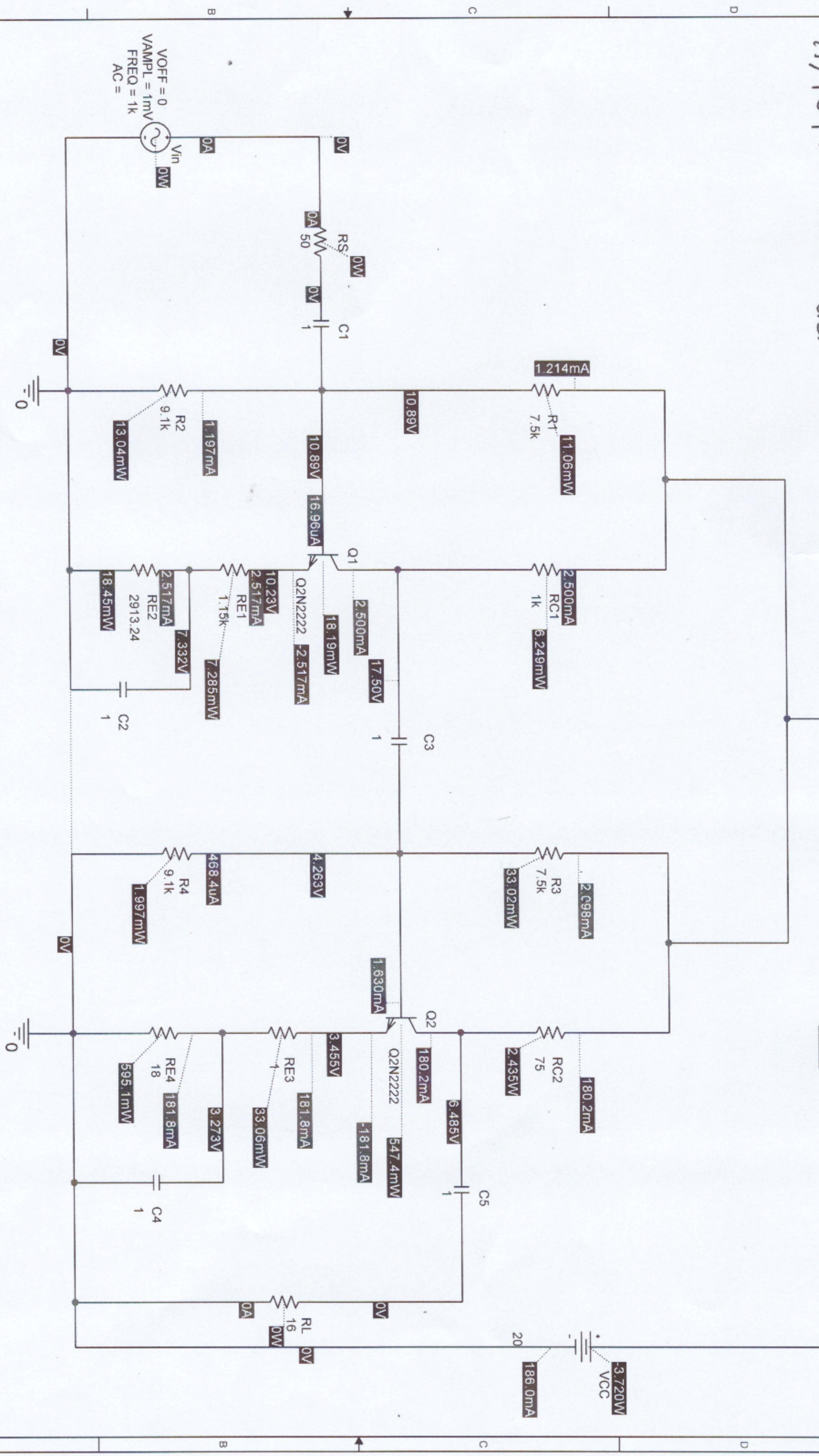

A

Title

Title		<Title>	
Size		Document Number	
A	<Doc>	Sheet	1 of 1

5

4

63

N

1

1

## PSpice part

### B) SIMULATED DC BIAS

Power amp stage (Project#1)

Simulated value	
ICQ	180.2mA
VCEQ	3.03V
VBEQ	0.808V
$P_D$ ,transistor	547.4mW


Simulated value		Hand-calculated value	
ICQ	2.5mA	ICQ	2.5mA
VCEQ	7.27V	VCEQ	7.3V
VBEQ	0.66V	VBEQ	0.7V
$P_D$ ,transistor	18.19mW	$P_{Ds}$ ,transistor	18.25mW

### C) SIMULATED POWER SUPPLY BIAS

DC power Supply Current (Ips) = 186mA.

It is less than 225mA. Thus, my circuit operate below the specification for maximum current, 225mA.
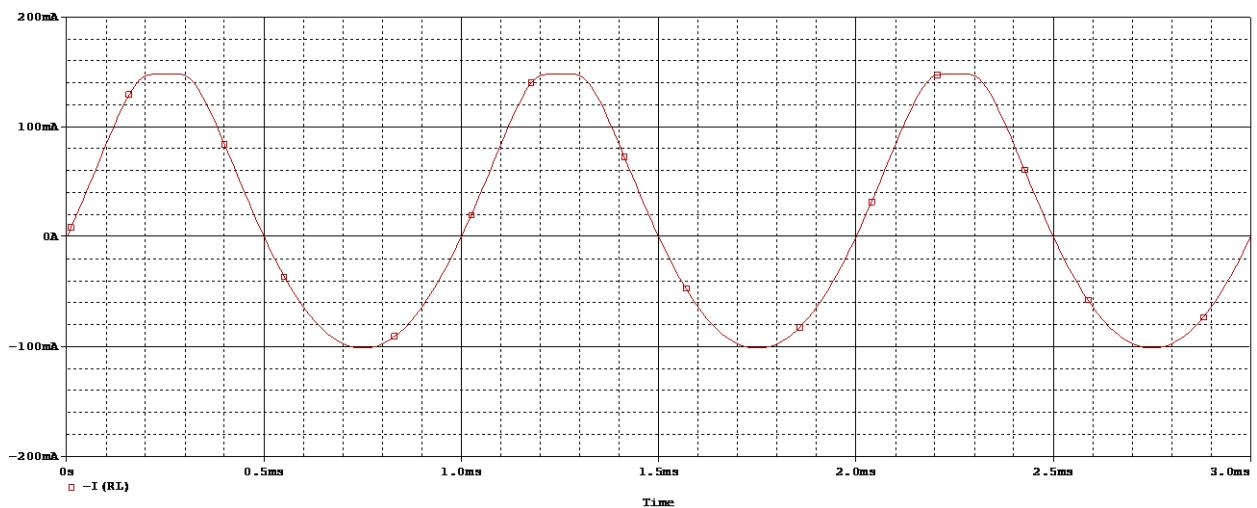
### D) SIMULATED CURRENT SWING ( $\beta=200$ )



It is clipping to 148 mA at the top. The small value of two value is 102mA.

The peak-to-peak swing in the output current,  $i_L$  = 204mA. So, my design does not achieve the 250mA peak-peak swing.

#### E) SIMULATED CURRENT SWING ( $\beta=100$ and $\beta=300$ )

Table for peak-to-peak swing in the output current,  $i_L$

$\beta=100$	$\beta=200$	$\beta=300$
168mA	204mA	60mA

Thus, my design does not achieve 125mA peak-to-peak swing under all conditions.

#### F) SIMULATED EFFICIENCY

$$PS = (V_{cc})(I_{ps}) = 20V * 0.186mA = 3.72W$$


$$PL = \left(\frac{i_L}{\sqrt{2}}\right)^2 (RL) = (0.0884)^2(16) = 0.125W$$

$$\eta = \frac{PL}{PS} = \frac{0.125W}{3.72W} = 0.0336 = 3.36\%$$

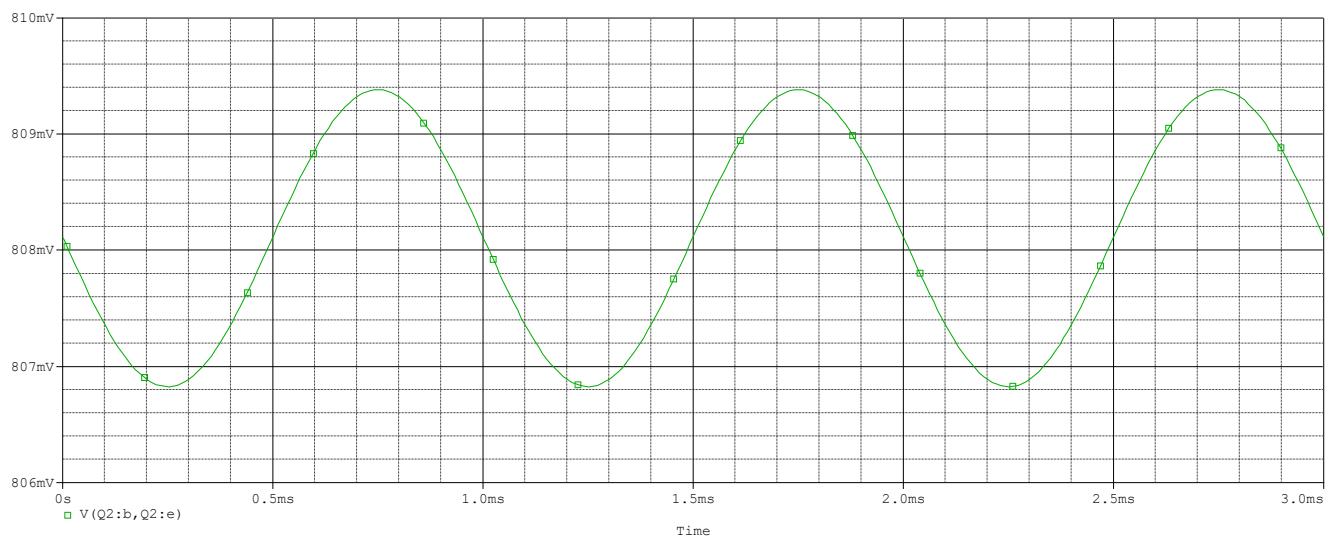
#### G) SIMULATED SMALL SIGNAL OPERATION

The amplitude value of the source voltage for small signal operation is 65mV for both transistors.

Power-amp stage transistor ( $\beta = 200$ )




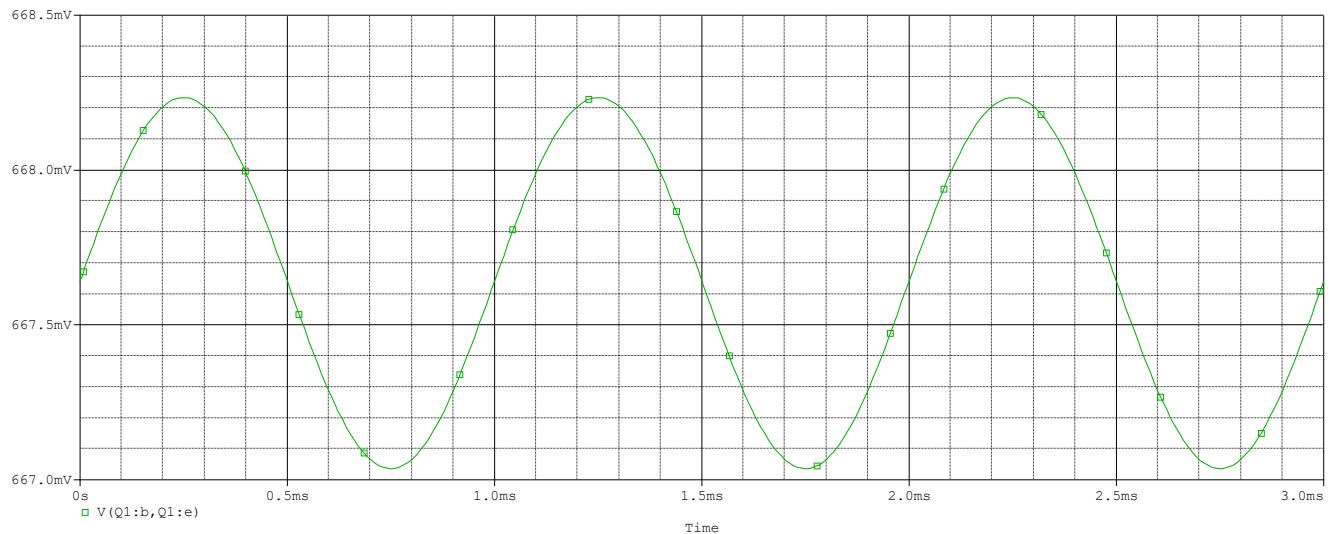Driver stage transistor ( $\beta = 200$ )


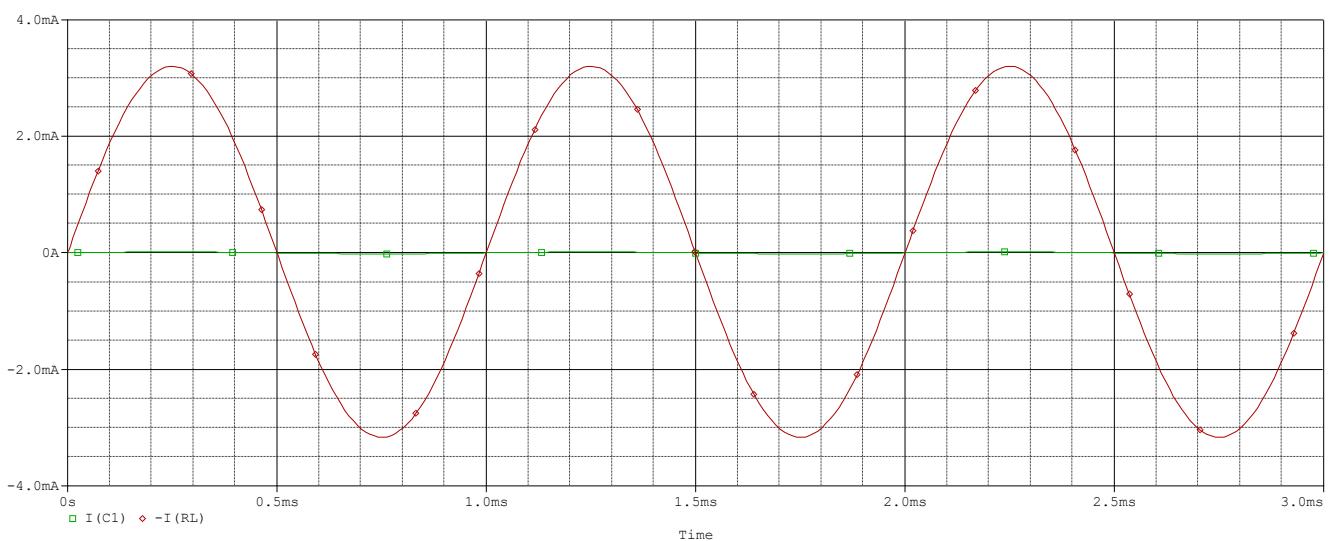
#### H) SIMULATED TWO-STAGE CURRENT GAIN

$$\beta = 200, A_i = \frac{3.2036mA}{15.975\mu A} = 200.54$$



Thus, I achieve a current gain, 200.

#### I) SIMULATED GAIN VARIATION WITH $\beta$

$$\beta = 100, A_i = \frac{2.2307mA}{16.234\mu A} = 137.41$$

$$\beta = 300, A_i = \frac{2.3346mA}{15.886\mu A} = 146.96$$

Table (Current gain)


$\beta=100$	$\beta=200$	$\beta=300$
137.41	200.54	146.96

$$\text{Percent gain variation} = \frac{200.54 - 200}{200} * 100 = 0.27\%$$

I achieve a current gain variation 15% about the nominal value of  $\beta = 200$ .
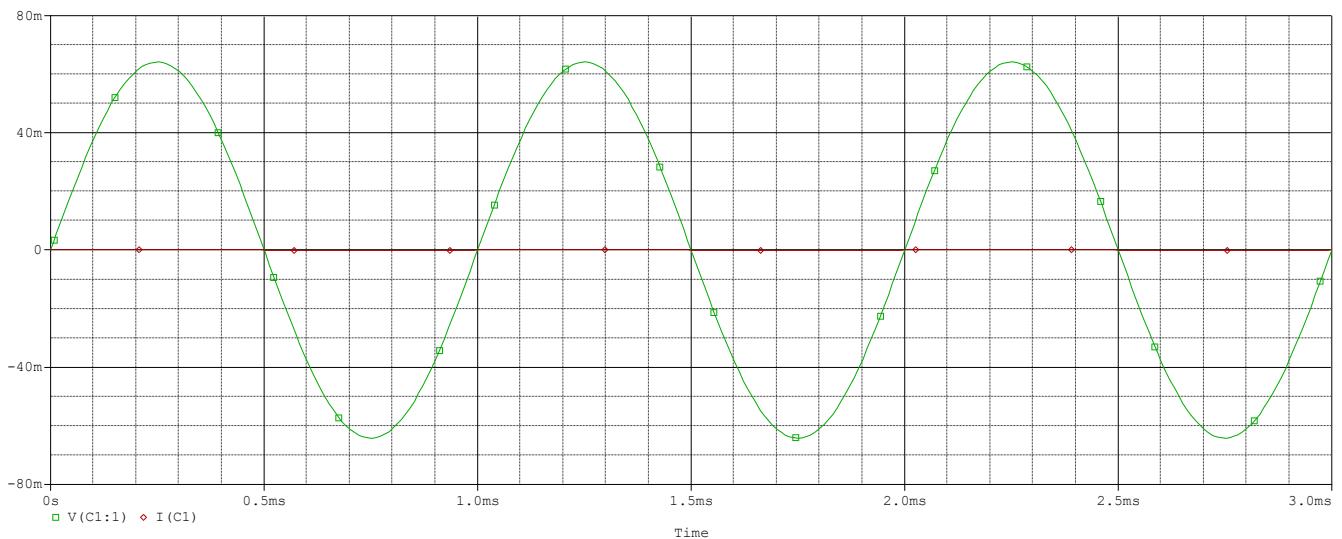
#### J) SIMULATED INPUT RESISTANCE

$$\beta = 200, R_{in} = \frac{64.198mV}{15.975\mu A} = 4018.65\Omega$$



$$\beta = 100, R_{in} = \frac{64.186mV}{16.234\mu A} = 3953.80\Omega$$


$$\beta = 300, R_{in} = \frac{64.202mV}{15.887\mu A} = 4041.17\Omega$$

$\beta = 100$	$\beta = 200$	$\beta = 300$
$3953.80\Omega$	$4018.65\Omega$	$4041.17\Omega$

I achieve an input resistance of less than  $10k\Omega$ .

## I) SIMULATED FREQUENCY RESPONSE


The 3dB bandwidth of the current gain =  $20 \log_{10} \left| \frac{i_L}{I_S} \right| = 20 \log_{10} |200.54| = 46.04$

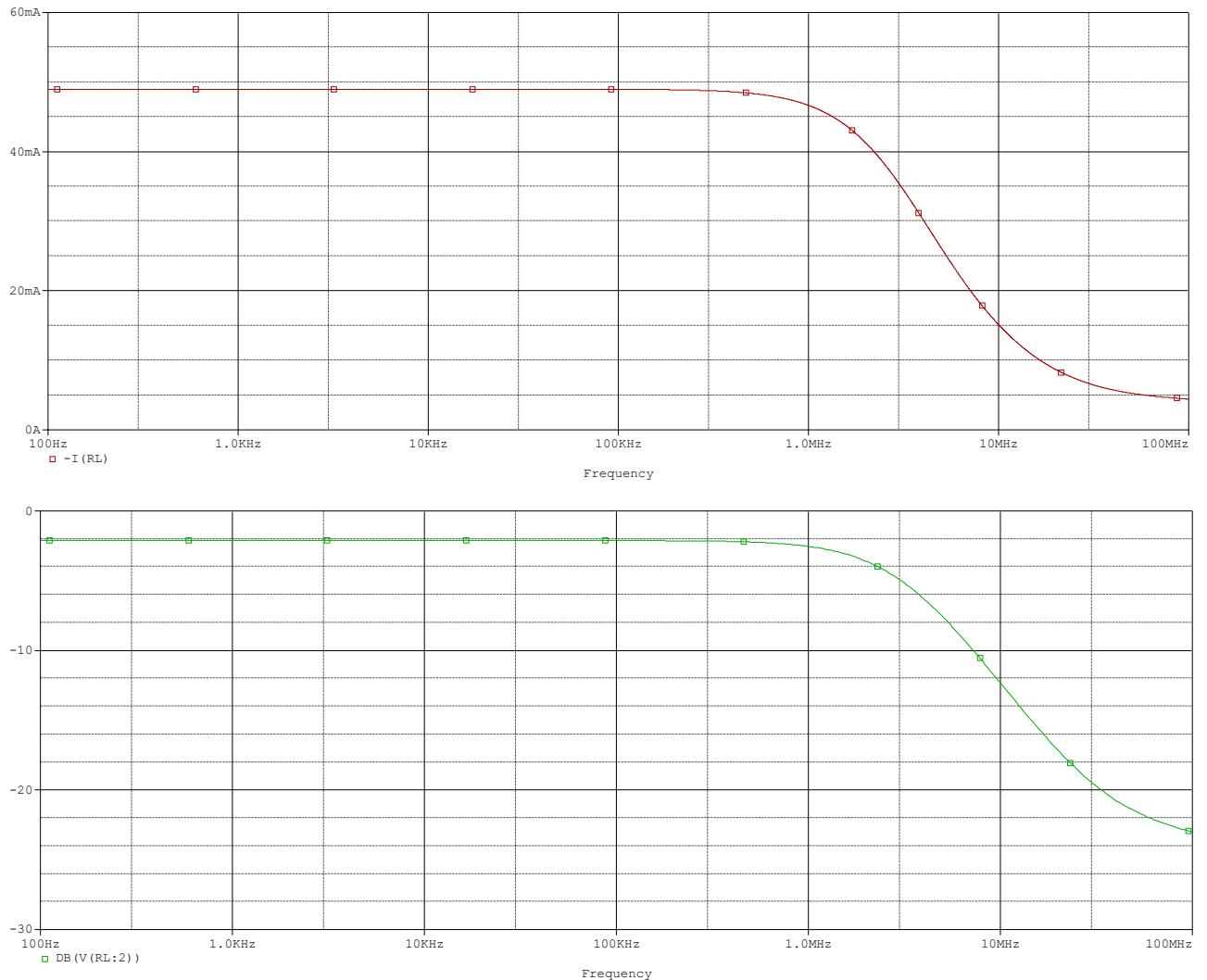

According to the graphs, it can be seen that -3dB is the cutoff frequency. Furthermore, this value is the point where the input voltage and current decrease by 0.707 times when delivered to the output.

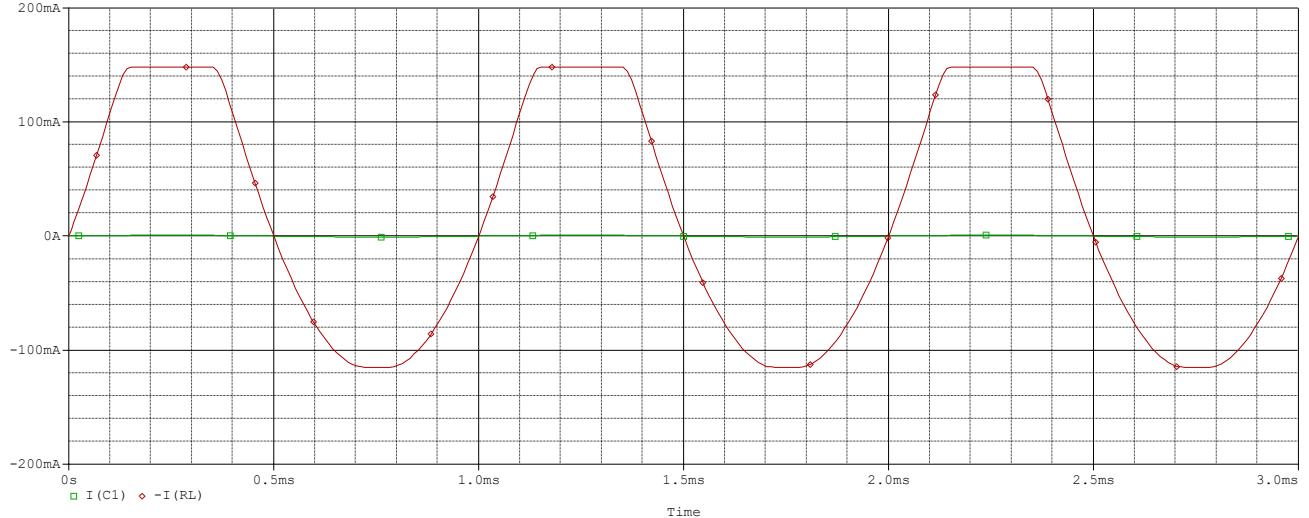
## J) SIMULATION USING STANDARD RESISTOR VALUES

The plot of  $i_L$  with clipping at both the positive and negative peaks using a  $\beta = 200$ .



The small value of two value is 115mA. The peak-to-peak swing in the output current,  $i_L = 230mA$ .

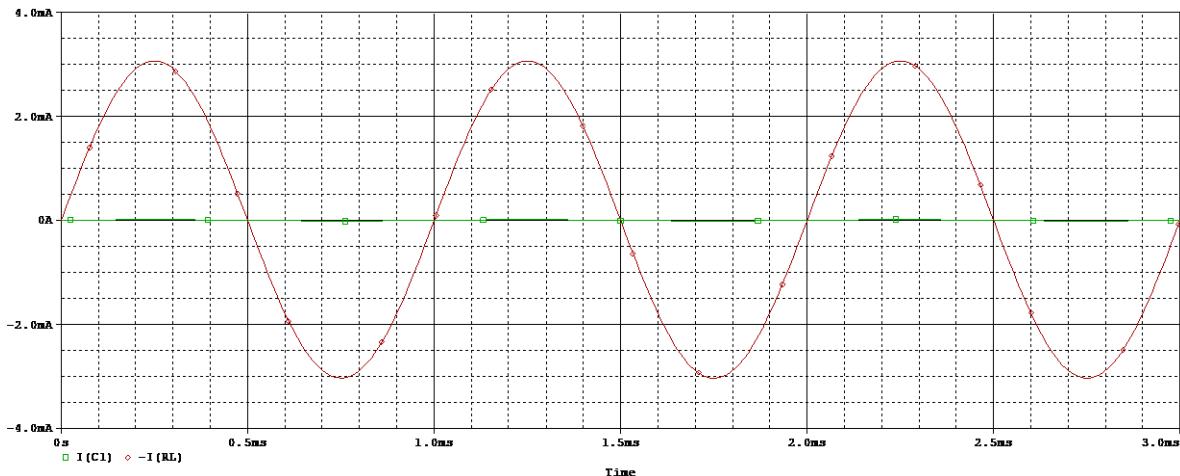The plots of  $i_S$  and  $i_L$  under small signal conditions



$$\beta = 200, Ai = \frac{3.0689mA}{15.959uA} = 192.28$$

$$\text{Percent gain variation} = \left| \frac{192.28 - 200}{200} * 100 \right| = 3.86\%$$

My design still achieves normal gain specifications when the resistors are changed. The total

peak to peak swing exceeds 250, but the bottom swing of the graph does not exceed 125mA.  
It seems that the offset is wrong.

Table (comparing the simulated peak swing, the simulated small signal gain and input resistance)

Original resistor

Peak swing	Small signal gain	Input resistance
204mA	200.54	$4018.65\Omega$

Standard resistor

Peak swing	Small signal gain	Input resistance
230mA	192.28	$4017.23\Omega$

BJT Power Amp and Driver Design: BOM (Project#1 and Project#2)

Name: \_\_\_\_\_Jaeha Huh\_\_\_\_\_

Lab Section: \_\_\_\_\_ C1LB\_\_\_\_\_

Note 1 – Resistor values, and power ratings should be chosen from standard resistor list.

## Note 2 – Enter the quantity of capacitors

Note 3 – Enter resistor values in ascending order.

Note 4 – Do not include RS, RL, 1Ω precision resistors.

Note 5 –Email this list to your lab TA.